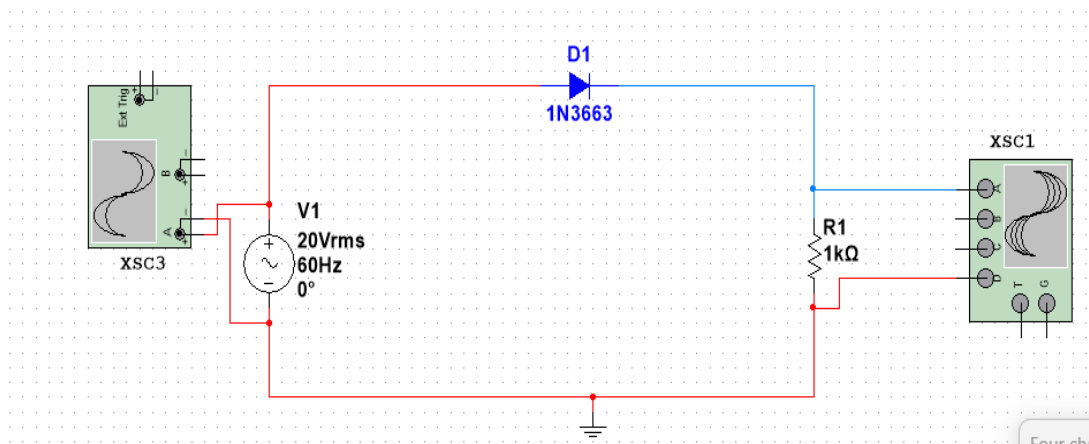
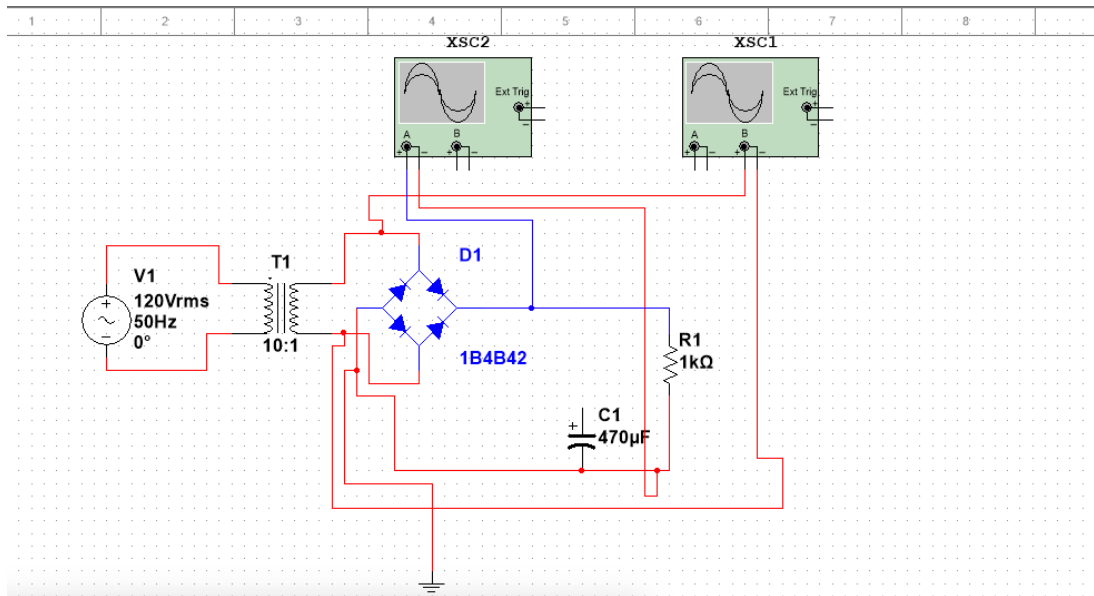


## Multisim Work:

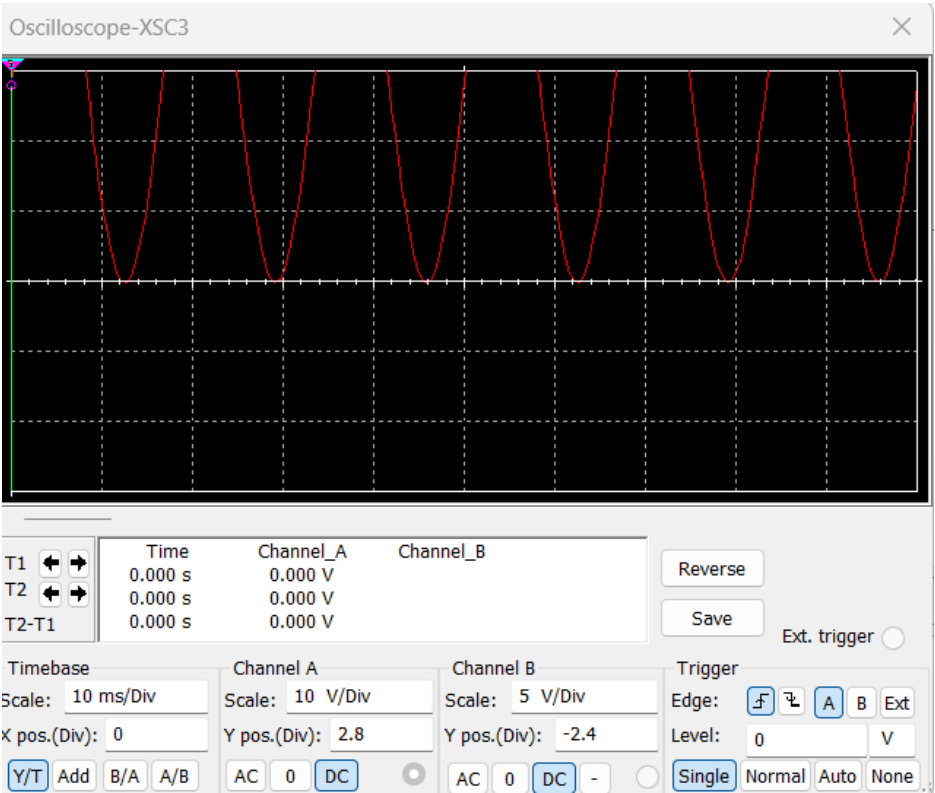


**Fig 3.1 Half-Wave Rectifier Circuit Diagram**

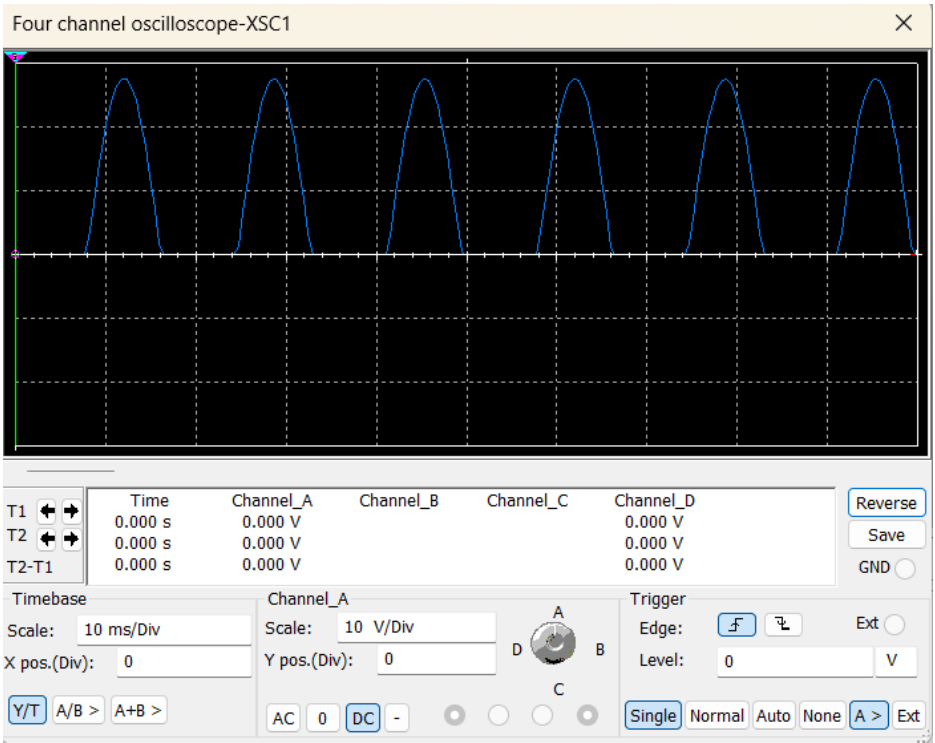


**Fig 3.2 Full-Wave Rectifier Circuit Diagram**


**Graphs:**




**Fig 3.3 Half-Wave Rectifier Circuit Diagram Graph**



**Fig 3.4 Half-Wave Rectifier Circuit Diagram Graph**

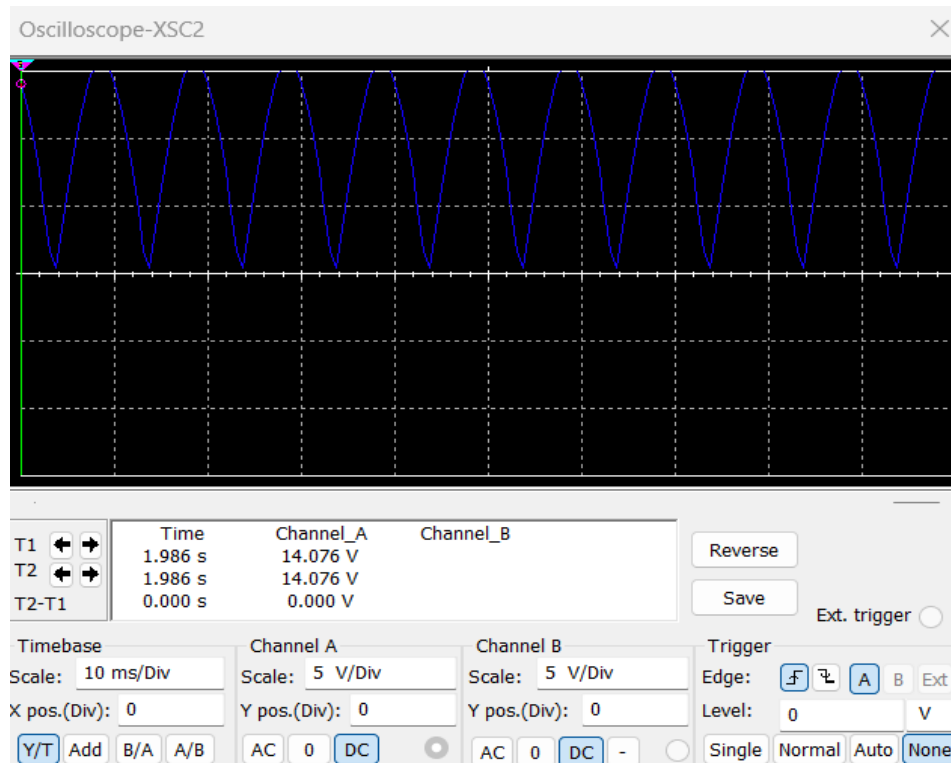

**Fig 3.5 Full-Wave Rectifier Circuit Diagram Graph**

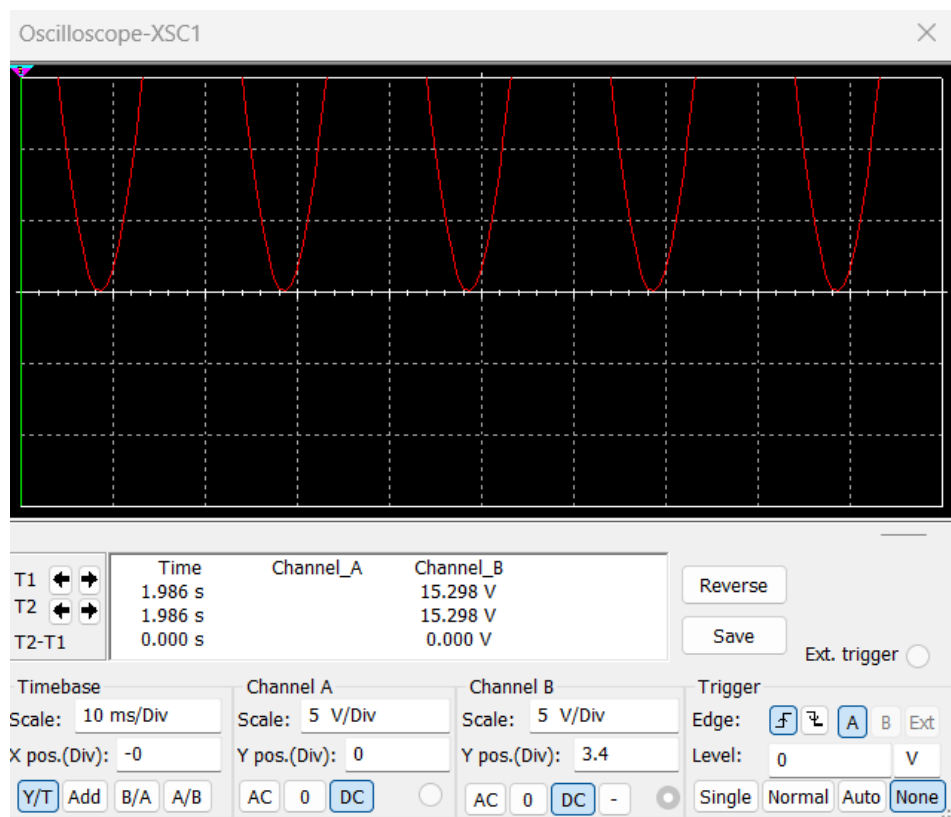

**Fig 3.6 Full-Wave Rectifier Circuit Diagram Graph**

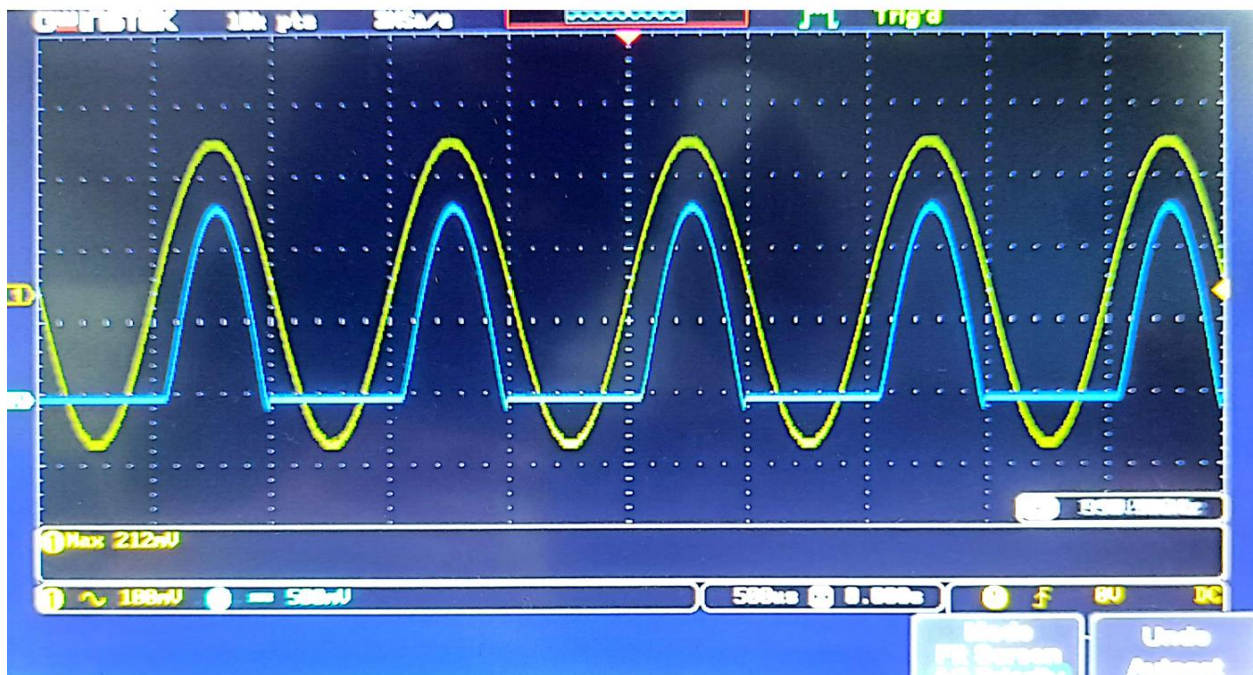


Fig 3.10 Half-Wave Rectifier Circuit Diagram Graph in Lab Oscillator

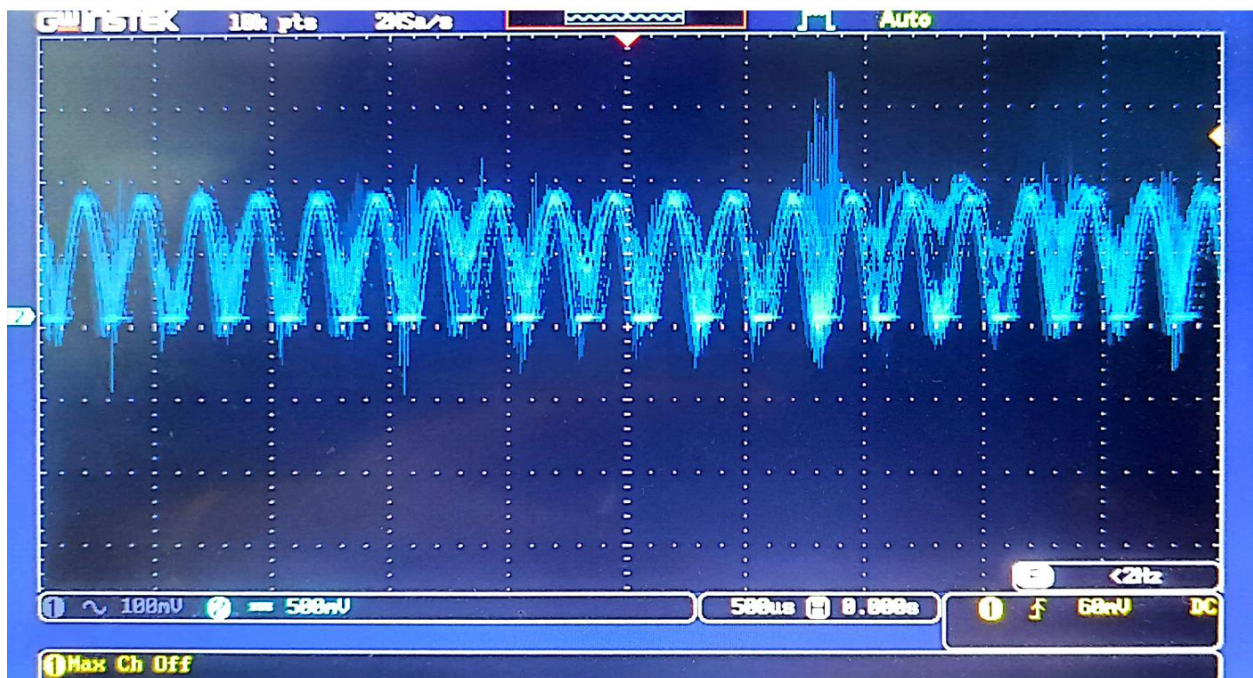


Fig 3.11 Full-Wave Rectifier Circuit Diagram Graph in Lab Oscillator

